

Noah Khan

April 22, 2022

8-Bit Full Adder

Description:

For this lab, I used multiplexers to implement combinational logic. I organized my logic using bit vectors (buses) in Verilog. This circuit added 0-3 to an 8-bit binary number and displayed the sum on the two right most digits on the seven-segment display. The logic utilized switches 0 – 7, btnL and btnC. Where the switches display the 8-bit digit and btnL/btnC adds to the 8-bit number.

Methods:

I began by creating the 3 multiplexer modules: x8 2-to-1, 4-to-1, and an 8-to-1. All of these modules used similar logic. Where S_0 represents the select lines and the F represents the output depending on the select line value.

Next, I created the full adder module. This module inherited the 4-to-1 module twice. Similar to Lab 2. The first instance took {cin, ~cin, ~cin, cin} as the input, {a, b} for the select lines, and s for the output. The second instance took {1'b1, cin, cin, 1'b0} as the input, {a, b} for the select lines, and cout for the output. This, I believe create a single bit adder. The diagram used can be found in appendix B (notes).


Next, I created the incrementer module. This module carried the task of being a ripple carry 8-bit adder. Where the full adder module was instantiated 8 times. Each of their “a” input was a bit from the 8-bit “a” vector. For the first 2 instances, b was b[0] and b[1] for the respective adders. For the first adder, cin was a 0 bit and for the rest it was cout from the preceding adder. Each adder output a bit into the 8-bit s vector, the bit’s index corresponded with the number of the adder.

The second to last module created was the hex7seg. This module was responsible for the LEDs displayed on the seven-segment. The truth table used was the same as the truth table in Lab 2.

The final module was the top-level module, which calls the incrementer, hex7seg twice, and the 8x 2-to-1 modules. In addition, this module was in charge of turning on the appropriate LEDs on the seven-segment board.

Results:

Design:

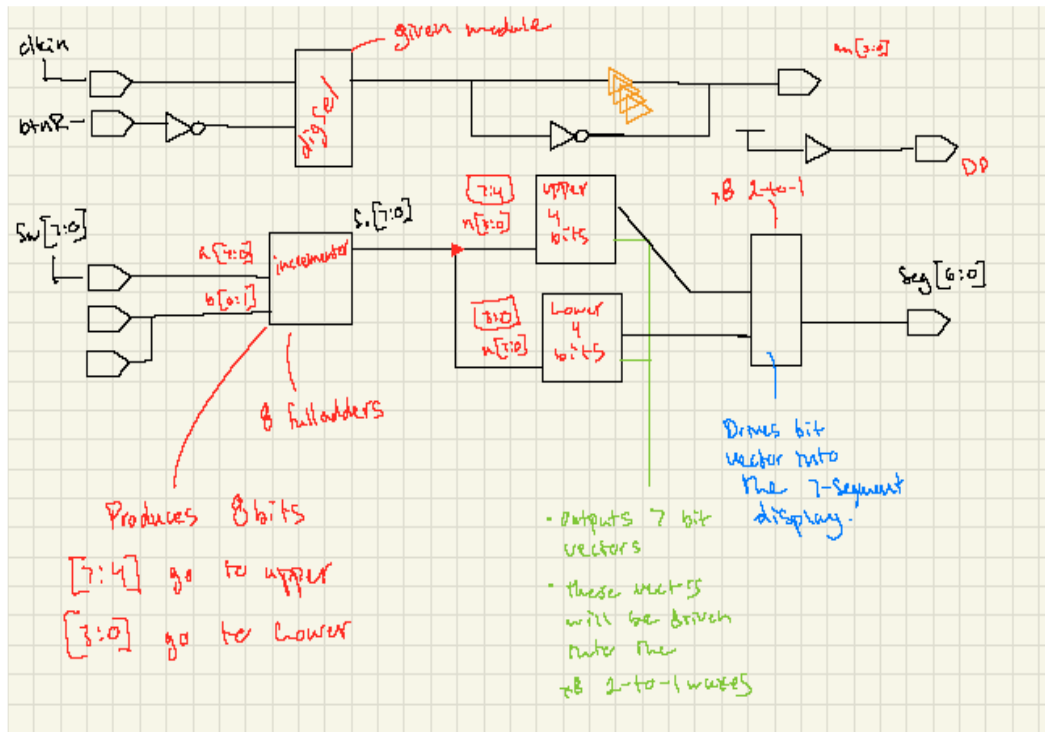

2-to-1 Truth Table

S ₀	F
0	I ₀
1	I ₂

Boolean Expression

$$I_0 \sim S + I_1 S$$

This is the logical expression for the 2-to-1 truth table. Where the \sim represents “not.” The other modules followed the same logic. The number of inputs will always be 2 to the power of the number of select lines. The logic is similar with the higher input multiplexers.

Hex7seg Truth Table

n3	n2	n1	n0	CA	CB	CC	CD	CE	CF	CG
0	0	0	0	0	0	0	0	0	0	1
0	0	0	1	1	0	0	1	1	1	1
0	0	1	0	0	0	1	0	0	1	0
0	0	1	1	0	0	0	0	1	1	0
0	1	0	0	1	0	0	1	1	0	0
0	1	0	1	0	1	0	0	1	0	0
0	1	1	0	0	1	0	0	0	0	0
0	1	1	1	0	0	0	1	1	1	1
1	0	0	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	1	1	0	0
1	0	1	0	0	0	0	1	0	0	0
1	0	1	1	1	1	0	0	0	0	0
1	1	0	0	0	1	1	0	0	0	1
1	1	0	1	1	0	0	0	0	1	0
1	1	1	0	0	1	1	0	0	0	0
1	1	1	1	0	1	1	1	0	0	0

Where n_{3-1} were used for the select lines and n_0 was used to determine whether the segment was on or off for a certain digit. Diagrams can be found in appendix B (notes).

I designed a single module at a time and got inspiration from Lab 2.

Testing & Simulation:

I tested my design by creating a testbench that tests the top-level module, similar to Lab 2. For this testbench, I created several test cases to test whether the switches output the appropriate number. I chose these inputs because they covered all the cases from 0000 0000 – FFFF FFFF. I believe there were a few corner cases, these cases include the btnL and btnC buttons. I checked to see the buttons worked individually, together and if they generated overflow. There were no problems that I can recall.

Lab Questions:

The dig_sel was oscillating at a frequency of 3.05 kHz.

I did not notice any flickering on the seven-segment display.

Conclusion:

From this lab, I learned how to use multiplexers for combinational logic, utilize bit vectors and display numbers on the seven-segment display. I encountered a few difficulties while doing this lab. I had an issue with my logic for my full adder, hex7seg and my incrementer. For my full adder, I originally used “a” for the input instead of c_{in} . For the incrementer I had the wrong inputs and outputs. I did not properly utilize all the inputs and outputs for this module at first. I later went back and changed the logic around. For the hex7seg module, I had the right idea for the logic, but it was backwards. I had to rearrange the inputs for the 8-to-1 mux. If I could redo this lab, I would test each module individually. Doing this would have saved me time. There aren’t any components that come to mind when I think of optimization.

Appendix Ax8 2-to-1 Multiplexer

```

`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 04/11/2022 07:38:24 PM
// Design Name:
// Module Name: m2_1
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////

module m2_1(
    input [7:0] in0,
    input [7:0] in1,
    input sel,
    output [7:0] o
);

    assign o[0] = (in0[0] & ~sel) | (in1[0] & sel);
    assign o[1] = (in0[1] & ~sel) | (in1[1] & sel);
    assign o[2] = (in0[2] & ~sel) | (in1[2] & sel);
    assign o[3] = (in0[3] & ~sel) | (in1[3] & sel);
    assign o[4] = (in0[4] & ~sel) | (in1[4] & sel);
    assign o[5] = (in0[5] & ~sel) | (in1[5] & sel);
    assign o[6] = (in0[6] & ~sel) | (in1[6] & sel);
    assign o[7] = (in0[7] & ~sel) | (in1[7] & sel);

endmodule

```

4-to-1 Multiplexer

```

`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 04/11/2022 07:10:50 PM
// Design Name:
// Module Name: m4_1
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////

module m4_1(
    input [3:0] in ,
    input [1:0] sel,
    output o
);

    assign o = (in[0] & ~sel[1] & ~sel[0]) | (in[1] & ~sel[1] & sel[0]) | (in[2] &
sel[1] & ~sel[0]) | (in[3] & sel[1] & sel[0]);

endmodule

```

8-to-1 Multiplexer

```

`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 04/11/2022 07:10:50 PM
// Design Name:
// Module Name: m8_1
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////

module m8_1(

    input [7:0] in,
    input [2:0] sel,
    output o

);

    assign o = (in[0] & ~sel[2] & ~sel[1] & ~sel[0]) | (in[1] & ~sel[2] & ~sel[1] &
sel[0]) | (in[2] & ~sel[2] & sel[1] & ~sel[0]) | (in[3] & ~sel[2] & sel[1] & sel[0])
| (in[4] & sel[2] & ~sel[1] & ~sel[0]) | (in[5] & sel[2] & ~sel[1] & sel[0]) |
(in[6] & sel[2] & sel[1] & ~sel[0]) | (in[7] & sel[2] & sel[1] & sel[0]);

endmodule

```

Full Adder

```

`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 04/11/2022 10:39:10 PM
// Design Name:
// Module Name: fulladder
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////

module fulladder(
    input a,
    input b,
    input cin,
    output cout,
    output s
);

    m4_1 m1 ( .in({cin, ~cin, ~cin, cin}), .sel({a, b}), .o(s) );
    m4_1 m2 ( .in({1'b1, cin, cin, 1'b0}), .sel({a, b}), .o(cout) );

endmodule

```

Incrementer


```

`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 04/11/2022 07:28:59 PM
// Design Name:
// Module Name: Incrementer
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////

module Incrementer(
    input [7:0] a0,
    input [1:0] b0,
    output [7:0] s0
);

    wire [7:0] c0;

    fulladder fa0 (.a(a0[0]), .b(b0[0]), .cin(1'b0), .cout(c0[0]), .s(s0[0]) );
    fulladder fa1 (.a(a0[1]), .b(b0[1]), .cin(c0[0]), .cout(c0[1]), .s(s0[1]) );
    fulladder fa2 (.a(a0[2]), .b(1'b0), .cin(c0[1]), .cout(c0[2]), .s(s0[2]) );
    fulladder fa3 (.a(a0[3]), .b(1'b0), .cin(c0[2]), .cout(c0[3]), .s(s0[3]) );
    fulladder fa4 (.a(a0[4]), .b(1'b0), .cin(c0[3]), .cout(c0[4]), .s(s0[4]) );
    fulladder fa5 (.a(a0[5]), .b(1'b0), .cin(c0[4]), .cout(c0[5]), .s(s0[5]) );
    fulladder fa6 (.a(a0[6]), .b(1'b0), .cin(c0[5]), .cout(c0[6]), .s(s0[6]) );
    fulladder fa7 (.a(a0[7]), .b(1'b0), .cin(c0[6]), .cout(c0[7]), .s(s0[7]) );

endmodule

```

Hex7seg

```

`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 04/12/2022 01:47:15 PM
// Design Name:
// Module Name: hex7seg
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////

module hex7seg(
    input [3:0] n,
    output [6:0] seg_out

);

    wire not_n0;
    assign not_n0 = ~n[0];

    m8_1 sevensegment0(.sel(n[3:1]), .in({1'b0, n[0], n[0], 1'b0, 1'b0, not_n0,
1'b0, n[0]}), .o(seg_out[0]));
    m8_1 sevensegment1(.sel(n[3:1]), .in({1'b1, not_n0, n[0], 1'b0, not_n0, n[0],
1'b0, 1'b0}), .o(seg_out[1]));
    m8_1 sevensegment2(.sel(n[3:1]), .in({1'b1, not_n0, 1'b0, 1'b0, 1'b0, 1'b0,
not_n0, 1'b0}), .o(seg_out[2]));
    m8_1 sevensegment3(.sel(n[3:1]), .in({n[0], 1'b0, not_n0, n[0], n[0], not_n0,
1'b0, n[0]}), .o(seg_out[3]));
    m8_1 sevensegment4(.sel(n[3:1]), .in({1'b0, 1'b0, 1'b0, n[0], n[0], 1'b1, n[0],
n[0]}), .o(seg_out[4]));
    m8_1 sevensegment5(.sel(n[3:1]), .in({1'b0, n[0], 1'b0, 1'b0, n[0], 1'b0, 1'b1,
n[0]}), .o(seg_out[5]));
    m8_1 sevensegment6(.sel(n[3:1]), .in({1'b0, not_n0, 1'b0, 1'b0, n[0], 1'b0,
1'b0, 1'b1}), .o(seg_out[6]));

```

Top-Level

```

`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 04/11/2022 08:45:23 PM
// Design Name:
// Module Name: Top_Level
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////


module Top_Level(
    input [7:0] sw,
    input btnL,
    input btnC,
    input btnR,
    input clkin,
    output [6:0] seg,
    output dp,
    output [3:0] an
);

    wire dig_sel;
    wire [7:0] inc_out;
    wire [6:0] seg_out1;
    wire [6:0] seg_out2;


    assign an[3] = 1'b1;
    assign an[2] = 1'b1;
    assign dp = 1'b1;
    assign an[0] = ~dig_sel;
    assign an[1] = dig_sel;

```


Elaborated Design

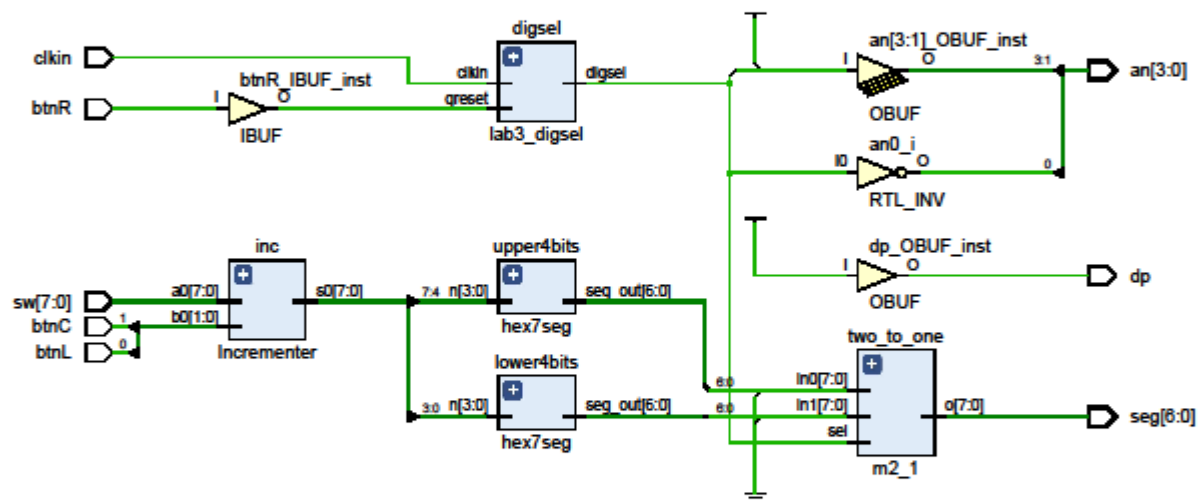

Simulation

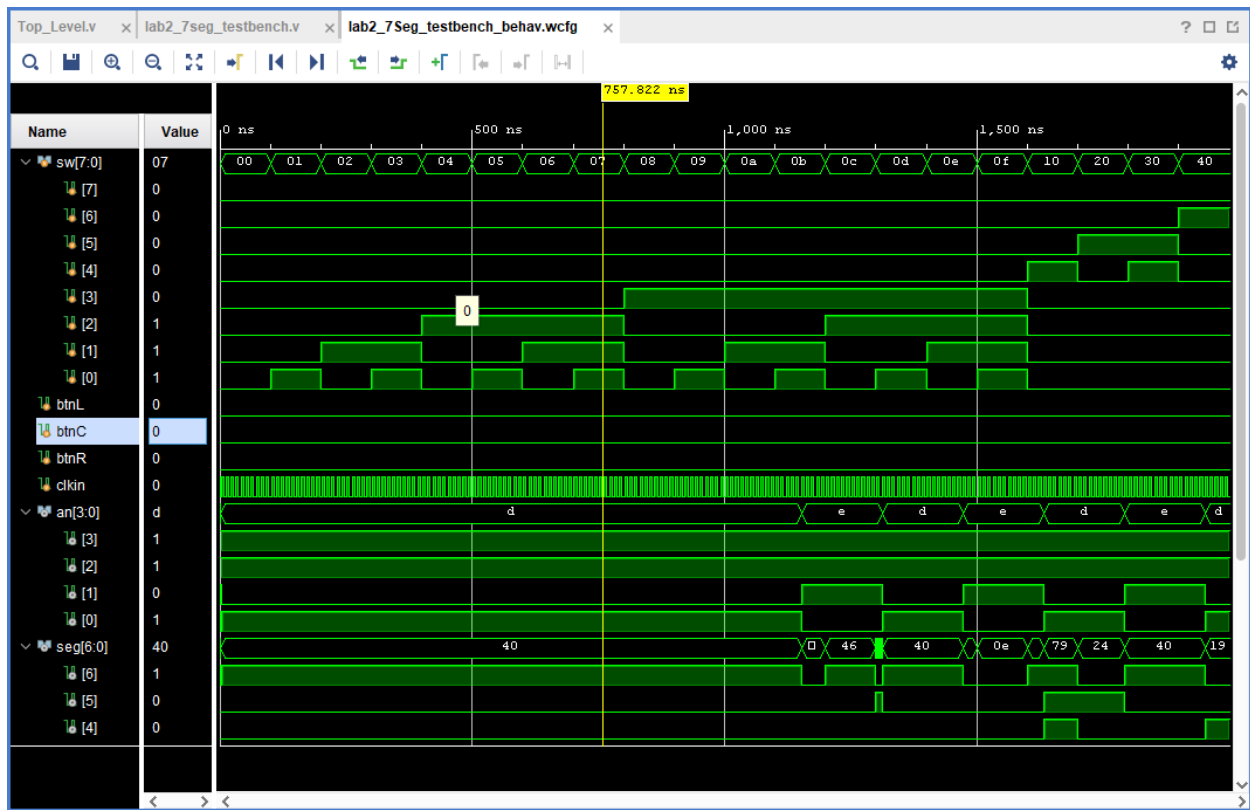

Waveform

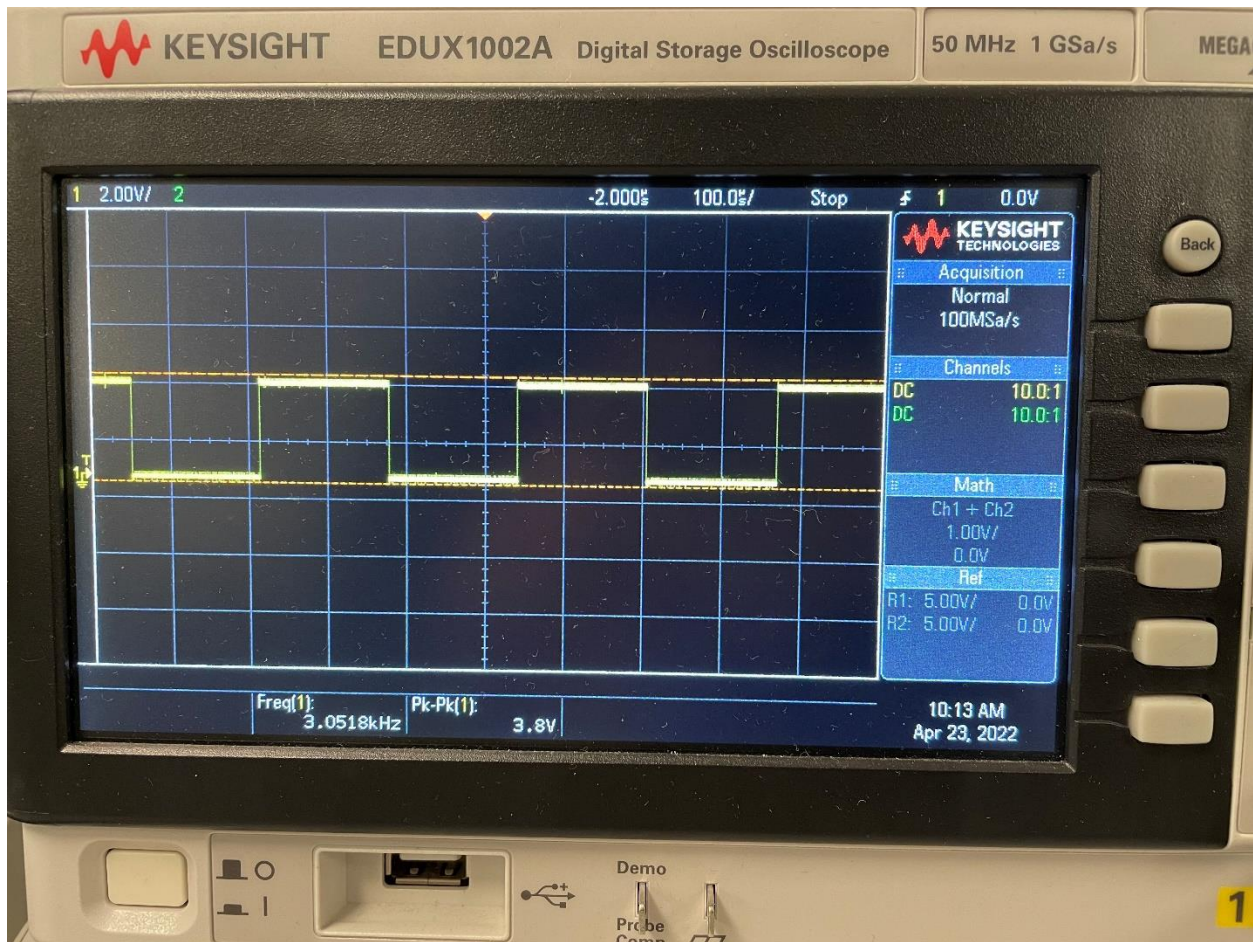


Appendix B (notes):

Lab 3 16 Apr 22 12:56 AM *Bus* 0.6
1000

Lab 3

but and butP
we switched


4-to-1 multiplexer T-table

 

S_1	S_0	f
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

2-to-1 Logic Gates (mux)

$$I_0 \bar{S} + I_1 S$$

 


$$I_0 \bar{S} + I_1 S$$

what do I need?

4-to-1 Logic Gates (mux)

Index[]

 

$$S_1 S_0 = 00$$

$$S_1 S_0 = 01$$


$$S_1 S_0 = 10$$

$$S_1 S_0 = 11$$

Most Significant bit and index is on the left

8-to-1 Mux

S_2, S_1, S_0

 

S_2	S_1	S_0	f
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
1	0	0	I_4
1	0	1	I_5
1	1	0	I_6
1	1	1	I_7

$$I_0 \bar{S}_2 \bar{S}_1 \bar{S}_0 + I_1 \bar{S}_2 \bar{S}_1 S_0 + I_2 \bar{S}_2 S_1 \bar{S}_0 + I_3 \bar{S}_2 S_1 S_0$$

$$I_4 S_2 \bar{S}_1 \bar{S}_0 + I_5 S_2 \bar{S}_1 S_0 + I_6 S_2 S_1 \bar{S}_0 + I_7 S_2 S_1 S_0$$


- Every instance has same port name
- Top level uses different wires to connect to ports

4-to-1 boolean Expression


$$I_0 \bar{S}_1 \bar{S}_0 + I_1 \bar{S}_1 S_0 + I_2 S_1 \bar{S}_0 + I_3 S_1 S_0$$

8-bit Adder - obtain Sum $S[7:0]$

 - Ripple Carry using Full adders
- 8 Full adders
- Full Adder
 - 2 4-to-1 multiplexers "M4_1"
 - One inverter
 - 0 and 1 as needed




geeksforgeek.org

 

$$m_1 = \{a, \bar{a}, \bar{a}, a\}$$

$$m_2 = \{0, a, a, 1\}$$

 



\overline{A}
 $F) \overline{a} | B$
 $E) \overline{c}$

7-Segment Always active low

	n_3	n_2	n_1	n_0	CA	CB	CC	CD	CE	CF	CG
0	0	0	0	0	0	0	0	0	0	0	1
1	0	0	0	1	1	0	0	1	1	1	1
2	0	0	1	0	0	0	1	0	0	1	0
3	0	0	1	1	0	0	0	0	1	1	0
4	0	1	0	0	1	0	0	1	1	0	0
5	0	1	0	1	0	1	0	0	1	0	0
6	0	1	1	0	0	1	0	0	0	0	0
7	0	1	1	1	0	0	0	1	1	1	1
8	1	0	0	0	0	0	0	0	0	0	0
9	1	0	0	1	0	0	0	1	1	0	0
10	1	0	1	0	0	0	0	1	0	0	0
11	1	0	1	1	1	1	0	0	0	0	0
12	1	1	0	0	0	1	1	0	0	0	1
13	1	1	0	1	1	0	0	0	0	1	0
14	1	1	1	0	0	1	1	0	0	0	0
15	1	1	1	1	0	1	1	1	0	0	0

- why so many multiplexers?
- How are the Multiplexers Suppose to be connected?
- what are the inputs?
-

Active low
meaning
0 is ON

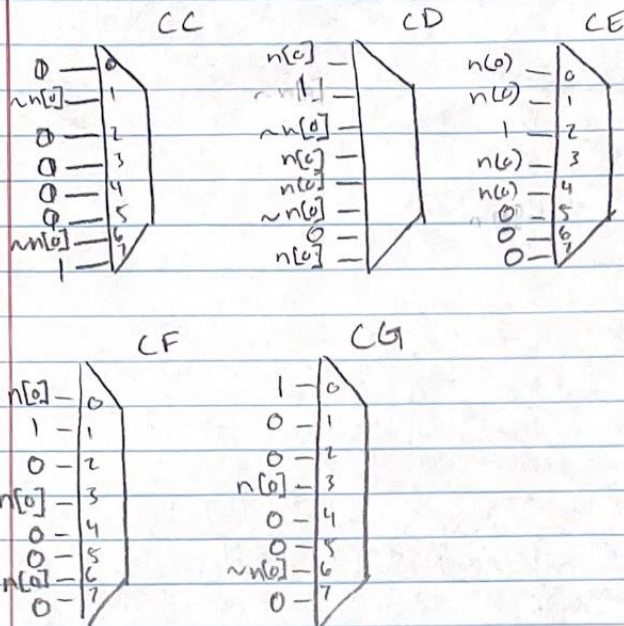 

$m0_1 [6:0] (.in(n[0]),$

Created my 8 inputs for the 7 muxes,
is there an easier way to drive
them?

Can I do it in a single line of
code rather than 7 different ones?



Full Adder

A	B	Cin	S	Cont
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

