

Noah Khan

May 6, 2022

16-Bit Hexadecimal Counter

Description:

For this lab, I created a sequential circuit using the library module FDRE for flip-flops. Completing this lab required 9 different modules. These modules are a 4-bit counter, 16-bit counter, selector, ring counter, edge detector, hex7seg, x8 2-to-1 multiplexers, and a top level. In addition, I created a mystery box module which handled logic for the center button. Furthermore, the hex7seg and the x8 2-to-1 multiplexer is reused from lab 3.

Methods:

I began by creating the 4-bit counter module. It had 5 inputs and 3 outputs. The 5 inputs were clk, Up, Dw, LD, and Din, where Din is was a 4-bit vector. The outputs were Q, UTC, and DTC, where Q was a 4-bit vector. This module handles the logic to increment or decrement the number displayed on the seven-segment LED on the Basys 3 board. Additionally, this module instantiates the FDRE flip flop 4 times. The flip flops have the inputs .C, .CE, .D, .Q which represent the clock, count enable, D (flip flop input) value and Q (flip flop output) value, respectively.

UTC is 1 when all the bits in Q are 1 and DTC is 1 when all the bits in Q are 0. To take care of this, I assigned UTC to $\&Q$ and DTC to $\&(\sim Q)$. For UTC, the logic ANDs all the bits of Q together. This way, if all bits are 1, UTC will be 1. For DTC, the logic inverts all the bits in Q then ANDs them together. In this case, if all the bits are 0, they will be inverted, ANDed together, and DTC will equal 1.

I created a wire named clk_enable. This wire will feed into CE, the count enable. I realized I made a mistake in naming the wire, it should be named count_enable. In any case, it transfers the proper logic, which is Dw XOR'd with Up and all of that is OR'd with LD.

Next, I created a 4-bit bus. This bus handles the addition and subtraction logic. Each wire from the bus feeds into one flip flop. I looked through the textbook and found helpful information for the addition logic. Then, I drew up some expressions that could possibly handle the subtraction logic. I OR'd these logical expressions together. I assigned each wire to their respective expressions.

After creating the 4-bit counter, I created the 16-bit counter. This module was similar to the 4-bit counter and instantiated the 4-bit counter 4 times. UTC and DTC used the same logic as the 4-bit counter.

After the creating the 16-bit counter, I created logic for the selector. From what I understood, H needed to equal the hex number indicated by the select value.

Afterwards, I created the ring counter. The schematic of this logical component could be found in the textbook. It requires 4 FDRE flip flops two inputs, clk and advance, and a 4-bit vector output [3:0] Qout. Where the .C port takes the clk input, .CE takes advance and the first flip flop takes the Qout[3] for .D and Qout[0] for the .Q port. The other flip flops have the same cascading logic. All their .R ports will be 0 and all of them will be initialized to 0 except for one of the flip flops. The one that is 1 is arbitrary.

Next was the edge detector, which had 2 inputs; clk and btn, and 1 output; y. In addition, it instantiates 2 FDRE flip flops Where the first takes btn for the .D port. There needs to be wires connecting .Q ports and .D port for the second flip flop.


Next, I created a mystery box module. This module was not necessary because the logic could be implemented into the top-level module. However, I did this for cleanliness. This module had a 16-bit vector as the input and btnC. The output can have any name. I named it "out." I inverted all the 14 most left bits for the 16-bit vector and OR'd the bits all together, then, I AND'd it with the btnC.

Finally, I created the top-level module. This module had 7 inputs, clkin, btnR, btnU, btnD, btnC, btnL, and a 16-bit vector sw. It had 4 outputs a 7-bit vector seg, dp, 4-bit vector an, and 16-bit vector led. I created an instance for mystery box, 2 for edge detector, ring counter, 16-bit counter, selector, hex7seg and lab4_clks, which was given in the lab manual. I connected all instances together while using the diagram in the lab manual as reference. I connected each index of "an" to each index of the output from the ring counter and inverted it. The logic I used for dp utilized index 1 and 2 for the ring counter output. Index 2 was AND'd with the UTC output and that was OR'd with index 1 and AND'd with the DTC output and the entire expression was negated.

I created a testbench for the lower-level modules to make sure they functioned properly.

Results:

Design:

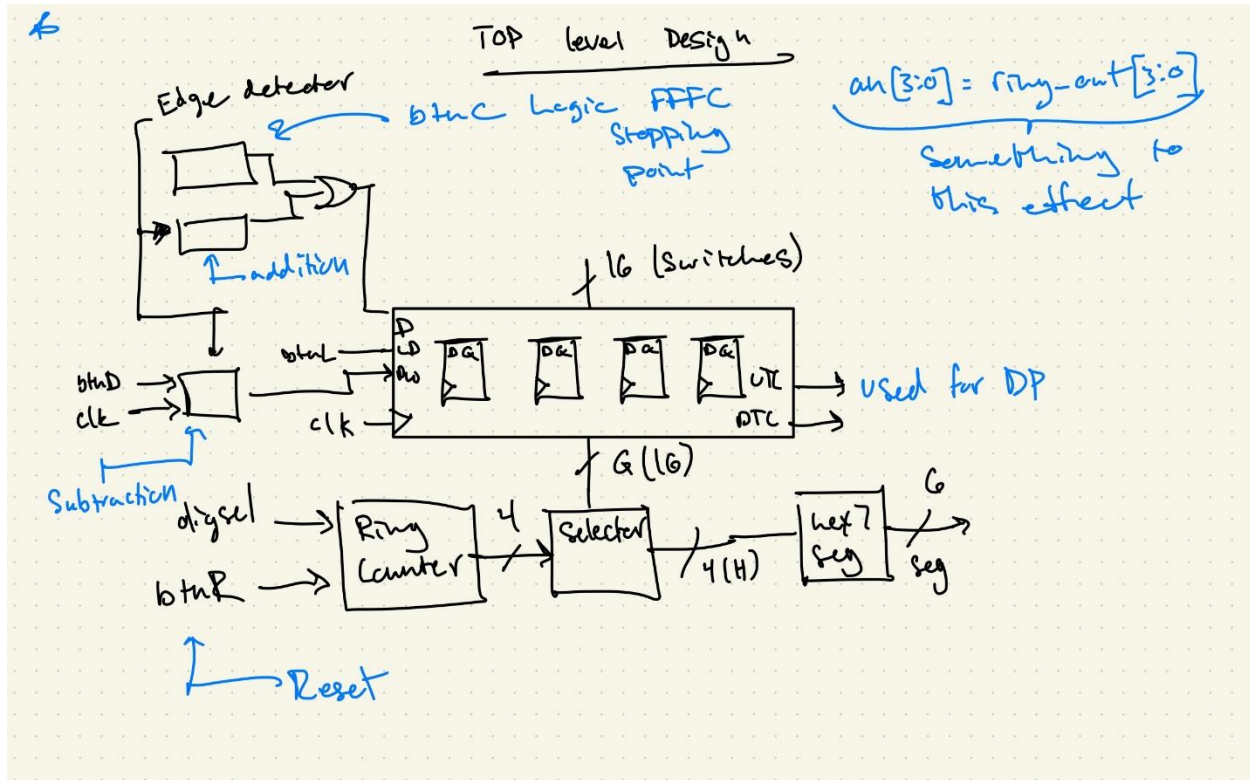

Testing & Simulation:

I created a testbench for most of the lower-level modules in lab 4. All simulations can be found in the lab submission file. The first module I tested was the 4-bit counter. I tested btnU, btnD, and btnL. I believe the test cases were making sure btnL worked while either btnU or btnD was on. In addition, I made sure UTC was 1 when all the bits were 1 and DTC was 1 when all the bits were 0.

The 16-bit counter was basically the same thing. However, while running simulations, I did notice there was an error with my load (btnL) logic. The right most hex number from Din would be loaded into all the Q values. This was fixed by changing some logic in the 16-bit counter module.

The ring counter was fairly simple, I gave a value to the "advance" input and saw the bit shift.

The edge detector was simple too, I checked to see when the clock edge would rise.

For the selector, I tested random inputs to see what the outcome would be. It worked properly, by giving me the hex number depending on the switch (0001, 0010, 0100, 1000) that was active.

I used the given testbench to test the top-level module.

I did not test the modules obtained from lab 3 and I did not test the mystery box module.

Lab Questions:

When I hold down btnR, all the LED segments on the seven-segment display turn off. I think this is because the lab 4 clks module handles the global reset which is mapped to btnR.

When fastclk is connected to the clock inputs instead of clk, I see an[2:0] are faint. I am assuming the segments are displaying for a short amount of time making the display seem faint.

Conclusion:

From this lab, I learned how to create a sequential circuit using FDRE flip flops. The hardest part for me was figuring out the logic for the 4 bit-counter and implementing it. A reoccurring problem for me was figuring out what the count enable input was for the other flip flops in the other modules. If I could do this lab again, would have gotten started on it earlier. I would not know how to optimize it.

Appendix A:

4-bit counter (1)

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 04/21/2022 03:42:26 PM
// Design Name:
// Module Name: countUD4L
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////

module countUD4L(
    input clk,
    input Up,          // increment
    input Dw,          // decrement
    input LD,          // load control
    input [3:0] Din,    // the 4-bit vector Din that will be loaded on the clock
    edge if LD is high.
    output [3:0] Q,      // current value held by the counter
    output UTC,          //1 only when the counter is at 1111 (Up Terminal Count)
    output DTC           //1 only when the counter is at 0000 (down Terminal Count)
);

    // TESTED
    assign UTC = &Q;
    assign DTC = &(~Q);

    wire [3:0]FF_wire;
    wire clk_enable;

    assign clk_enable = (Dw ^ Up) | LD;

    assign FF_wire[0] = (Q[0] ^ clk_enable);
    assign FF_wire[1] = ( Up & (Q[1] ^ (Q[0] & clk_enable))) | (Dw & (Q[1] ^ (~Q[0]
& clk_enable)));
```

4-bit counter (2)

```
    assign FF_wire[2] = ( Up & (Q[2] ^ (Q[1] & Q[0] & clk_enable))) | (Dw & (Q[2] ^
(~Q[1] & ~Q[0] & clk_enable)));
    assign FF_wire[3] = ( Up & (Q[3] ^ (Q[2] & Q[1] & Q[0] & clk_enable))) | (Dw
& (Q[3] ^ (~Q[2] & ~Q[1] & ~Q[0] & clk_enable)));

    FDRE #(.INIT(1'b0) ) ff_Q0 (.C(clk), .R(1'b0), .CE(clk_enable), .D( (LD &
Din[0]) | (~LD & FF_wire[0]) ), .Q(Q[0]));
    FDRE #(.INIT(1'b0) ) ff_Q1 (.C(clk), .R(1'b0), .CE(clk_enable), .D( (LD &
Din[1]) | (~LD & FF_wire[1]) ), .Q(Q[1]));
    FDRE #(.INIT(1'b0) ) ff_Q2 (.C(clk), .R(1'b0), .CE(clk_enable), .D( (LD &
Din[2]) | (~LD & FF_wire[2]) ), .Q(Q[2]));
    FDRE #(.INIT(1'b0) ) ff_Q3 (.C(clk), .R(1'b0), .CE(clk_enable), .D( (LD &
Din[3]) | (~LD & FF_wire[3]) ), .Q(Q[3]));

endmodule
```

16-bit counter (1)

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 04/26/2022 02:04:11 AM
// Design Name:
// Module Name: countUD16L
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////

module countUD16L(

    input clk,
    input Up, // increment
    input Dw, // decrement
    input LD, // load control
    input [15:0] Din, // the 4-bit vector Din that will be loaded on the clock edge
    if LD is high.
    output [15:0] Q, // current value held by the counter
    output UTC, //1 only when the counter is at 1111 (Up Terminal Count)
    output DTC //1 only when the counter is at 0000 (down Terminal Count)

);
// TESTED
assign UTC = &Q;
assign DTC = &(~Q);

    wire [3:0] utc_connect;
    wire [3:0] dtc_connect;

    countUD4L c0 ( .clk(clk), .Up(Up), .Dw(Dw), .LD(LD), .Din(Din[3:0]),
.Q(Q[3:0]), .UTC(utc_connect[0]), .DTC(dtc_connect[0]) );
    countUD4L c1 ( .clk(clk), .Up(Up & ~Dw & utc_connect[0]), .Dw(Dw & ~Up &
dtc_connect[0]), .LD(LD), .Din(Din[7:4]), .Q(Q[7:4]), .UTC(utc_connect[1]),
```

16-bit counter (2)

```
.DTC(dtc_connect[1]) );
    countUD4L c2 ( .clk(clk), .Up(Up & ~Dw & (&utc_connect[1:0])), .Dw(Dw & ~Up &
(&dtc_connect[1:0])), .LD(LD), .Din(Din[11:8]), .Q(Q[11:8]), .UTC(utc_connect[2]),
.DTC(dtc_connect[2]) );
    countUD4L c3 ( .clk(clk), .Up(Up & ~Dw & (&utc_connect[2:0])), .Dw(Dw & ~Up &
(&dtc_connect[2:0])), .LD(LD), .Din(Din[15:12]), .Q(Q[15:12]), .UTC(utc_connect[3]),
.DTC(dtc_connect[3]) );

endmodule
```


Edge Detector

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 04/26/2022 05:16:50 PM
// Design Name:
// Module Name: EdgeDetector
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////

module EdgeDetector(

    input clk,
    input btn,
    output y

);

    // TESTED i think it works, may have possible errors?

    wire [1:0] wires;

    FDRE #(.INIT(1'b0)) ffUp_0 (.C(clk), .CE(1'b1), .D(btn), .Q(wires[0]));
    FDRE #(.INIT(1'b0)) ffUp_1 (.C(clk), .CE(1'b1), .D(wires[0]), .Q(wires[1]));

    assign y = wires[0] & ~wires[1];

endmodule
```

Hex7seg

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 04/12/2022 01:47:15 PM
// Design Name:
// Module Name: hex7seg
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////

module hex7seg(
    input [3:0] n,
    output [6:0] seg_out
);
    wire not_n0;
    assign not_n0 = ~n[0];

    m8_1 sevensegment0(.sel(n[3:1]), .in({1'b0, n[0], n[0], 1'b0, 1'b0, not_n0,
1'b0, n[0]}), .o(seg_out[0]));
    m8_1 sevensegment1(.sel(n[3:1]), .in({1'b1, not_n0, n[0], 1'b0, not_n0, n[0],
1'b0, 1'b0}), .o(seg_out[1]));
    m8_1 sevensegment2(.sel(n[3:1]), .in({1'b1, not_n0, 1'b0, 1'b0, 1'b0, 1'b0,
not_n0, 1'b0}), .o(seg_out[2]));
    m8_1 sevensegment3(.sel(n[3:1]), .in({n[0], 1'b0, not_n0, n[0], n[0], not_n0,
1'b0, n[0]}), .o(seg_out[3]));
    m8_1 sevensegment4(.sel(n[3:1]), .in({1'b0, 1'b0, 1'b0, n[0], n[0], 1'b1, n[0],
n[0]}), .o(seg_out[4]));
    m8_1 sevensegment5(.sel(n[3:1]), .in({1'b0, n[0], 1'b0, 1'b0, n[0], 1'b0, 1'b1,
n[0]}), .o(seg_out[5]));
    m8_1 sevensegment6(.sel(n[3:1]), .in({1'b0, not_n0, 1'b0, 1'b0, n[0], 1'b0,
1'b0, 1'b1}), .o(seg_out[6]));

endmodule
```

x8 2-to-1 multiplexers

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 04/11/2022 07:10:50 PM
// Design Name:
// Module Name: m8_1
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////

module m8_1(

    input [7:0] in,
    input [2:0] sel,
    output o

);

    assign o = (in[0] & ~sel[2] & ~sel[1] & ~sel[0]) | (in[1] & ~sel[2] & ~sel[1] &
sel[0]) | (in[2] & ~sel[2] & sel[1] & ~sel[0]) | (in[3] & ~sel[2] & sel[1] & sel[0])
| (in[4] & sel[2] & ~sel[1] & ~sel[0]) | (in[5] & sel[2] & ~sel[1] & sel[0]) |
(in[6] & sel[2] & sel[1] & ~sel[0]) | (in[7] & sel[2] & sel[1] & sel[0]);

endmodule
```

Ring Counter

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 04/26/2022 04:21:52 PM
// Design Name:
// Module Name: RingCounter
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////

module RingCounter(
    input clk,
    input advance,
    output [3:0] Qout
);
    // TESTED
    FDRE #(.INIT(1'b0) ) ff_0 (.C(clk), .R(1'b0), .CE(advance), .D(Qout[3]),
    .Q(Qout[0]));
    FDRE #(.INIT(1'b0) ) ff_1 (.C(clk), .R(1'b0), .CE(advance), .D(Qout[0]),
    .Q(Qout[1]));
    FDRE #(.INIT(1'b0) ) ff_2 (.C(clk), .R(1'b0), .CE(advance), .D(Qout[1]),
    .Q(Qout[2]));
    FDRE #(.INIT(1'b1) ) ff_3 (.C(clk), .R(1'b0), .CE(advance), .D(Qout[2]),
    .Q(Qout[3]));

endmodule
```

Selector

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 04/26/2022 02:40:13 AM
// Design Name:
// Module Name: selector
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////

module selector(
    input [3:0] sel,
    input [15:0] N,
    output [3:0] H
);
    // TESTED
    assign H[0] = (sel[0] & N[0] ) | (sel[1] & N[4] ) | (sel[2] & N[8] ) | (sel[3] &
N[12]);
    assign H[1] = (sel[0] & N[1] ) | (sel[1] & N[5] ) | (sel[2] & N[9] ) | (sel[3] &
N[13]);
    assign H[2] = (sel[0] & N[2] ) | (sel[1] & N[6] ) | (sel[2] & N[10] ) | (sel[3] &
N[14]);
    assign H[3] = (sel[0] & N[3] ) | (sel[1] & N[7] ) | (sel[2] & N[11] ) | (sel[3] &
N[15]);

endmodule
```

Mystery Box

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 04/27/2022 03:38:01 PM
// Design Name:
// Module Name: MysteryBox
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////

module MysteryBox(
    input [15:0] Q,
    input btnC,
    //input clk,
    output out
);

    assign out = ~(Q[15:2])&btnC;

endmodule
```

Top-Level (1)

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 04/25/2022 08:55:52 PM
// Design Name:
// Module Name: Top_Level
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////

module Top_Level(

    input clkIn,          //- this is the 100MHz clock on the Basys 3 Board
    input btnR,            //- this button will be connected the built-in global reset
of the Artix 7 FPGA
    input btnU,            //- when pressed this button causes the counter to increment
by just one
    input btnD,            //- when pressed this button causes the counter to decrement
by just one
    input btnC,            //- when pressed this button causes the counter to advance
continuously except in the FFFC to FFFF range
    input btnL,            //- when pressed this button causes the counter to load the
value determined by the switches on the clock edge
    input [15:0] sw,        //- this 16 bit vector determines the value loaded into the
counter when btnL is pressed
    output [6:0] seg,       //- this 7 bit vector controls the segments in the
7-segment display
    output dp,              //- this controls the dp segments in the 7-segment
display. Remember: when value is UTC left center is lit and when value is DTC right
center is lit.
    output [3:0] an,        //- this 4 bit vector controls the 4 digits of
7-segment display
    output [15:0] led        //- this 16 bit output corresponds to the switches.
```

Top-Level (2)

```
);
// if issues occur, troubleshoot: ringcounter, selector, edge detector
wire [3:0] select_to_hex7;
wire [3:0] ring_to_selctor;
wire [15:0] count16_out;
wire digsel, clk, edge_up, edge_dw, mystery_to_count16, utc_wire, dtc_wire;

MysteryBox mb ( .Q(count16_out), .btnC(btnC), .out(mystery_to_count16) );
EdgeDetector egdeUp ( .clk(clk), .btn(btnU), .y(edge_up) );
EdgeDetector egdeDw ( .clk(clk), .btn(btnD), .y(edge_dw) );

RingCounter ring ( .clk(clk), .advance(digsel), .Qout(ring_to_selctor) );


countUD16L count16 ( .clk(clk), .Up(mystery_to_count16 | edge_up), .Dw(edge_dw),
.LD(btnL), .Din(sw), .Q(count16_out), .UTC(utc_wire), .DTC(dtc_wire));
selector sel ( .sel(ring_to_selctor), .N(count16_out), .H(select_to_hex7));
hex7seg seven_seg ( .n(select_to_hex7), .seg_out(seg) );

lab4_clks slowit (.clkin(clkin), .greset(btnR), .clk(clk), .digsel(digsel));

assign dp = ~((ring_to_selctor[2]&utc_wire)|(ring_to_selctor[1]&dtc_wire));
//an[2] is utc, an[1] is dtc
assign an[0] = ~ring_to_selctor[0];
assign an[1] = ~ring_to_selctor[1];
assign an[2] = ~ring_to_selctor[2];
assign an[3] = ~ring_to_selctor[3];
assign led[15:0] = sw[15:0];

endmodule
```


Waveform

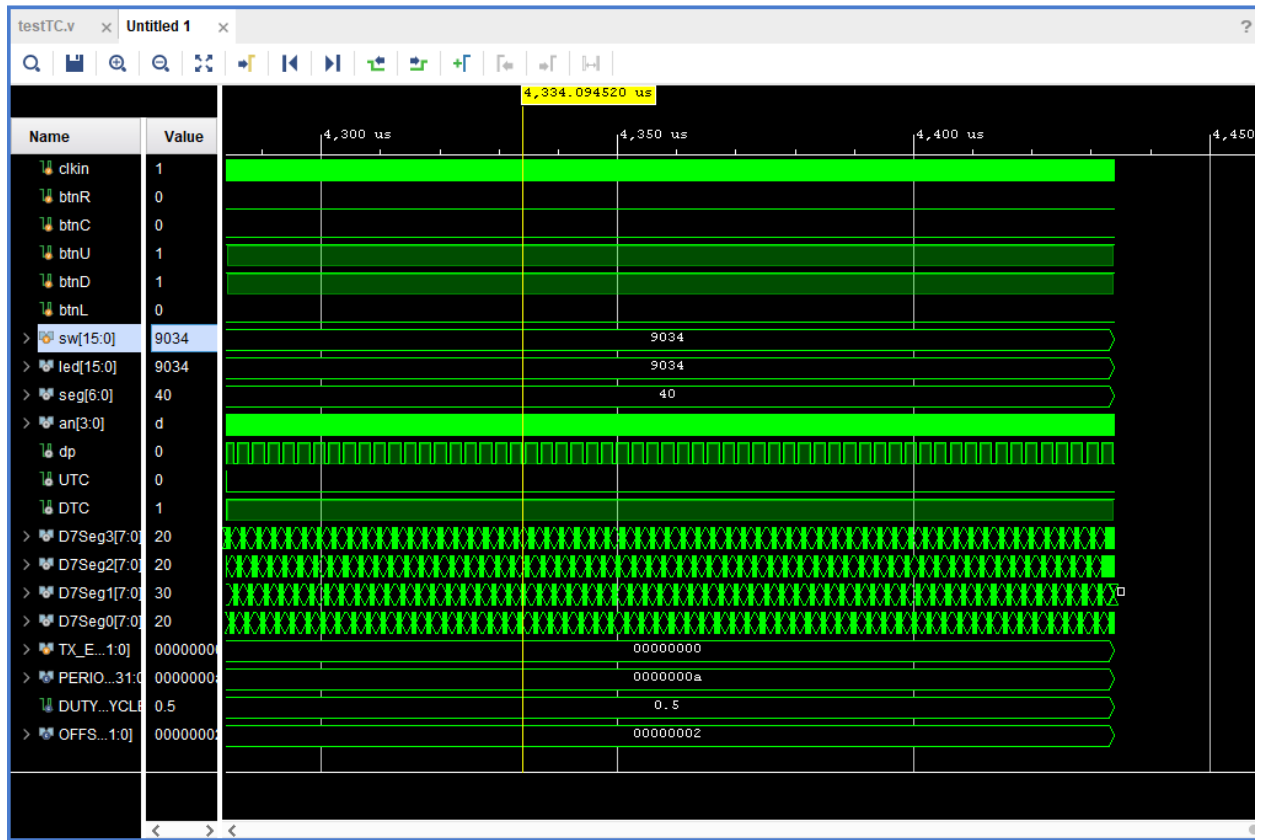

Appendix B:

Addition

*

if $UP = 1$ then

$$D_0 = Q_0 \oplus CE$$


$$D_1 = Q_1 \oplus Q_0 CE$$

$$D_2 = Q_2 \oplus Q_1 Q_0 CE$$

$$D_3 = Q_3 \oplus Q_2 Q_1 Q_0 CE \quad \text{--- } z$$

else

Current value

 

Subtraction

*

if $D_w = 1$

then do




else Q

$$D_0 = Q_0 \oplus CE$$

$$D_1 = Q_1 \oplus Q_0 CE$$

$$D_2 = Q_2 \oplus Q_1 Q_0 CE$$
 
$$D_3 = Q_3 \oplus Q_2 Q_1 Q_0 CE \quad \text{--- } z$$



Selector logic

✱

Selector

Boolean Expression



s_3	s_2	s_1	s_0	H
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1

$$\overline{s}_3 \overline{s}_2 \overline{s}_1 s_0 N[3:0] + \overline{s}_3 \overline{s}_2 s_1 \overline{s}_0 N[7:4]$$

$$\bar{s}_3 \bar{s}_2 \bar{s}_1 \bar{s}_0 N[11:8] + s_3 \bar{s}_2 \bar{s}_1 \bar{s}_0 N[15:12]$$

$$S_0 N[3:0] + S_1 N[7:4] +$$

$$S_2 N[11:0] + S_3 N[15:12]$$

Mystery box



Stop at FFFC Do not go further


Focus on the First 14 bits

↳ last 2 bits?

if $G[15:2] = 1$

then $\sim \text{btrc}$

else

 

$1 (\sim G[15:2]) \& \text{btrc}$